



**AMERICAN INTERNATIONAL UNIVERSITY – BANGLADESH**  
**Faculty of Engineering**

**Course Name:** Digital Logic and Circuits

**Deadline: 04/07/2023(Class time)**

**Semester:** Summer2022-23    **Term:** Mid    **Assignment:** 01    **Total Marks:** 10

**Question Mapping with Course Outcomes:**

Item	COs	POIs	K	P	A	Marks	Obtained Marks
Q1	CO1	P.a.2.C3	K2			10	
<b>Total:</b>						<b>10</b>	

**Student Information:**

**Student Name:**

**Student ID:**

**Section:**

**Department:**

**Submission Instruction:**

- Do not copy from others.
- Please print this page and write your answer in this page (Extra paper is not allowed)
- Write your **Name, ID, Subject & Section** properly
- **Last Date of Submission : 04.07.2023 (Class Time)**

1. Design a system that can be used in a safety push button lock device. There will be two switches. If the value of A is greater than B or A is equal to B, lock mechanism opens. In any other case the lock mechanism remains closed. Let's say X is the lock mechanism, construct a truth table of the system and design the logic circuit for the system using magnitude comparator block diagram and necessary gate/s. [10]